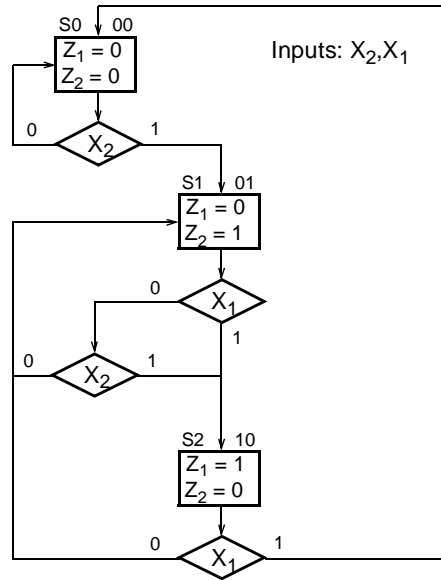


**Problem Solutions to Problems Marked With a * in
Logic Computer Design Fundamentals, Ed. 2**

CHAPTER 8

© 2000 by Prentice-Hall, Inc.


8-1.



8-2.

A:	0	1	1	0	1	1	
B:	1	1	1	1	0	0	
C:	0	1	0	1	0	1	
State:	ST1	ST1	ST2	ST3	ST1	ST2	ST3
Z:	0	0	1	1	0	0	

8-5.

 


Problem Solutions – Chapter 8

8-8.

$ST1(t + 1) = ST1 \cdot \bar{A} + ST2 \cdot B \cdot C + ST3$, $ST2(t + 1) = ST1 \cdot A$, $ST3(t + 1) = ST2 \cdot (\bar{B} + \bar{C})$, $Z = ST2 \cdot B + ST3$
 For the D flip-flops, $DST_i = ST_i(t + 1)$ and $ST_i = Q(ST_i)$. Reset initializes the flip-flops: $ST1 = 1$, $ST2 = ST3 = 0$.

8-9.

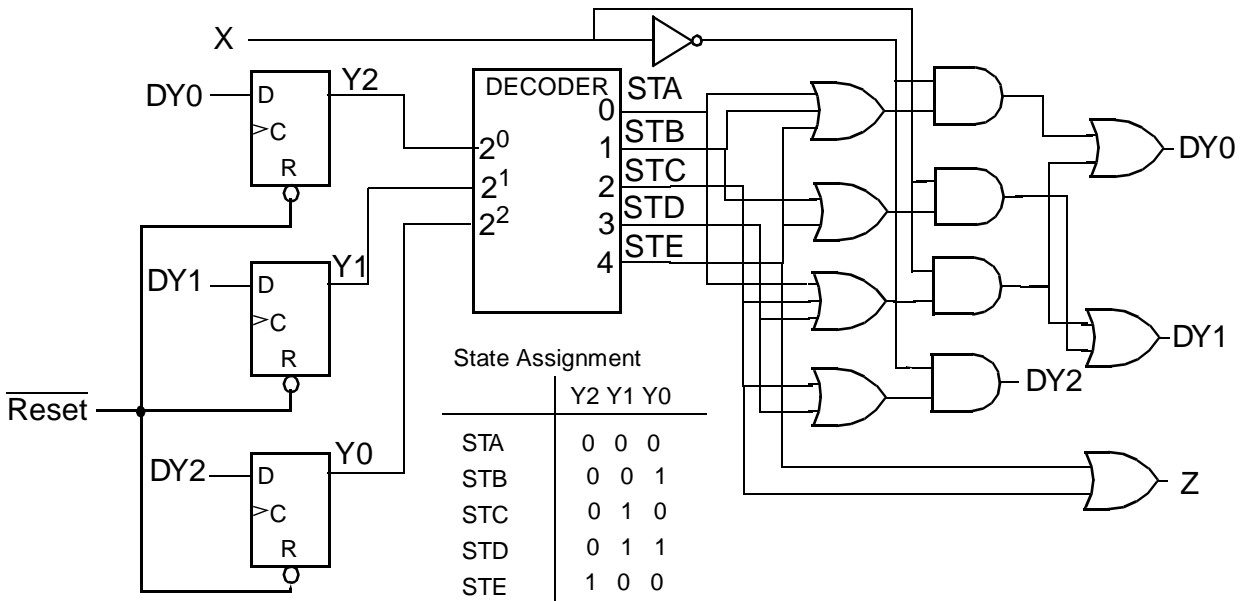

8-12.

```

    100110 (38)
    × 110101 (×53)
    -----
    100110
    000000
    100110
    000000
    100110
    100110
    -----
    11111011110 (2014)
    
```

```

    100110
    110101
    -----
    000000      Init PP
    100110      Add
    100110      After Add
    0100110     After Shift
    00100110   After Shift
    100110      Add
    10111110   After Add
    010111110  After Shift
    0010111110 After Shift
    100110      Add
    1100011110 After Add
    01100011110 After Shift
    100110      Add
    11111011110 After Add
    011111011110 After Shift
    
```


8-20.

```

library IEEE;
use IEEE.std_logic_1164.all;

entity asm_820 is
  port (
    A, B, C, CLK, RESET: in STD_LOGIC;
    Z: out STD_LOGIC
  );
end asm_820;


architecture asm_820_arch of asm_820 is
  type state_type is (ST1, ST2, ST3);
  signal state, next_state : state_type;
begin

  state_register: process (CLK, RESET)
  begin
    if RESET='1' then --asynchronous RESET active High
      state <= ST1;
    elsif (CLK'event and CLK='1') then --CLK rising edge
      state <= next_state;
    end if;
  end process;

  next_state_func: process (A, B, C, state)
  begin
    case (state) is
      when ST1 =>
        if A = '0' then
          next_state <= ST1;
        else
          next_state <= ST2;
        end if;
      when ST2 =>
        if ((B = '1') and (C = '1')) then
          next_state <= ST1;
        else
          next_state <= ST3;
        end if;
      when ST3 =>
        next_state <= ST1;
    end case;
  end process;

  --Output Z only depends on the state and input 'B'
  output_func: process (B, state)
  begin
    case (state) is
      when ST1 =>
        Z <= '0';
      when ST2 =>
        if (B = '1') then
          Z <= '1';
        else
          Z <= '0';
        end if;
      when ST3 =>
        Z <= '1';
    end case;
  end process;
end asm_820_arch;

```

 

NOTE: State hex value 4 corresponds to ST1, 2 to ST2 and 1 to ST3.

8-21. Errata: A, B, C should be ST1, ST2, ST3.

```


module asm_821 (CLK, RESET, A, B, C, Z);
input CLK, RESET, A, B, C;
output Z;
reg [1:0] state, next_state;
parameter ST1=2'b00, ST2=2'b01, ST3=2'b10, ST4=2'b11;
reg Z;

//State register
always @(posedge CLK or posedge RESET)
begin
if (RESET) //asynchronous RESET active High
state <= ST1;
else //use CLK rising edge
state <= next_state;
end

//Next state function
always @(A or B or C or state)
begin
case (state)
ST1: next_state <= A ? ST2: ST1;
ST2: next_state <= (B && C) ? ST1: ST3;
ST3: next_state <= ST1;
ST4: next_state <= ST1; // Next state ST1 is assigned to unused state ST4.
endcase
end


//Output function
always @(B or state)
begin
case (state)
ST1: Z <= 1'b0;
ST2: Z <= B ? 1'b1: 1'b0;
ST3: Z <= 1'b1;
ST4: Z <= 0'b0;
endcase
end
endmodule

```

 

NOTE: State hex value 0 cooresponds to ST1, 1 to ST2 and 2 to ST3.

8-28.

 

Total = 1024 words x 28 bits/word = 28,672 bits

8-32.

- a) Opcode = 8 bits , b) 16 bits c) 65,536 d) -32768 to +32767

Problem Solutions – Chapter 8

8-39. Errata: Problem 8-39(d): $C \leftarrow 0$ should be $C = 0$.

ADDR	NXT	MS	MC	IL	PI	PL	TD	TA	TB	MB	FS	MD	RW	MM	MW
a)	—	17	NXT	NXA	NLI	NLP	DR	SA	SB	Register	$F = A - B$	FnUt	WR	—	NW
	—	17	001	0	0	0	0	0	0	0	00101	0	1	0	0
DR = 3, SA = 1, SB = 2															
b)	—	—	CNT	—	NLI	NLP	DR	SA	—	Register	$F = \text{lsr } A$	FnUt	WR	—	NW
	—	—	000	0	0	0	0	0	0	0	10100	0	1	0	0
DR = 5, SA = 5															
c)	—	21	BNZ	NXA	NLI	NLP	—	—	—	—	—	—	—	—	—
	—	21	111	0	0	0	0	0	0	0	00000	0	0	0	0
DR = 5, SA = 5															
d)	—	—	CNT	—	NLI	NLP	DR	SA	—	Register	$F = A$	FnUt	WR	—	NW
	—	—	000	0	0	0	0	0	0	0	00000	0	1	0	0
DR = 6, SA = 6															

8-47.

Pipeline Fill	3 cycles
Execution Write-Backs	22 cycles
Final Register Load	1 cycle
TOTAL	26 cycles or $26 \times 5 = 130$ ns