

Fig. 2.1. Block Diagram of a Digital Computer

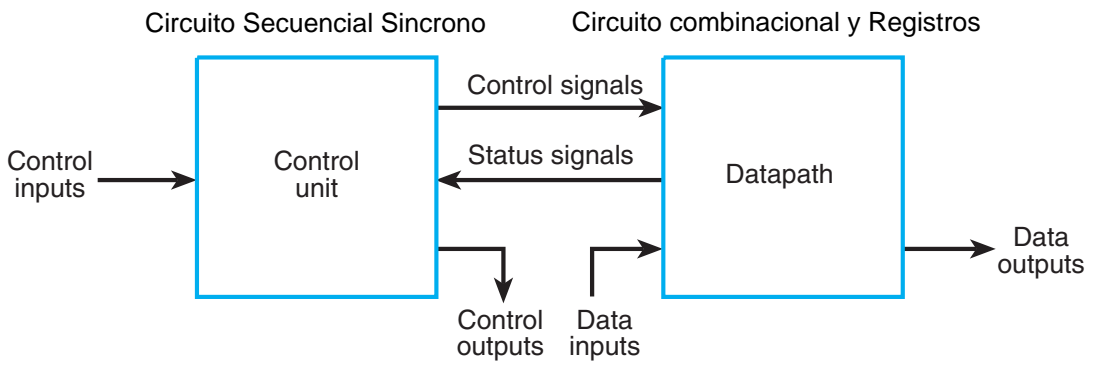


Fig. 2.2. Interaction between Datapath and Control Unit

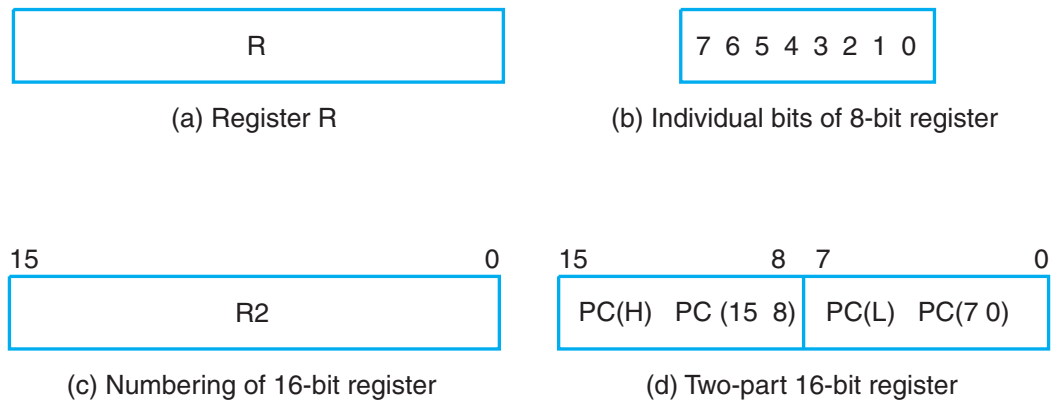


Fig. 2.3. Block Diagrams of Registers

2-3

Operador Reemplazo <-

$R2 \leftarrow R1$. Copia contenido R1 en R2 (R1 no se modifica)

Señal de control K_1

If ($K_1=1$) then ($R2 \leftarrow R1$)

$K_1: R2 \leftarrow R1$

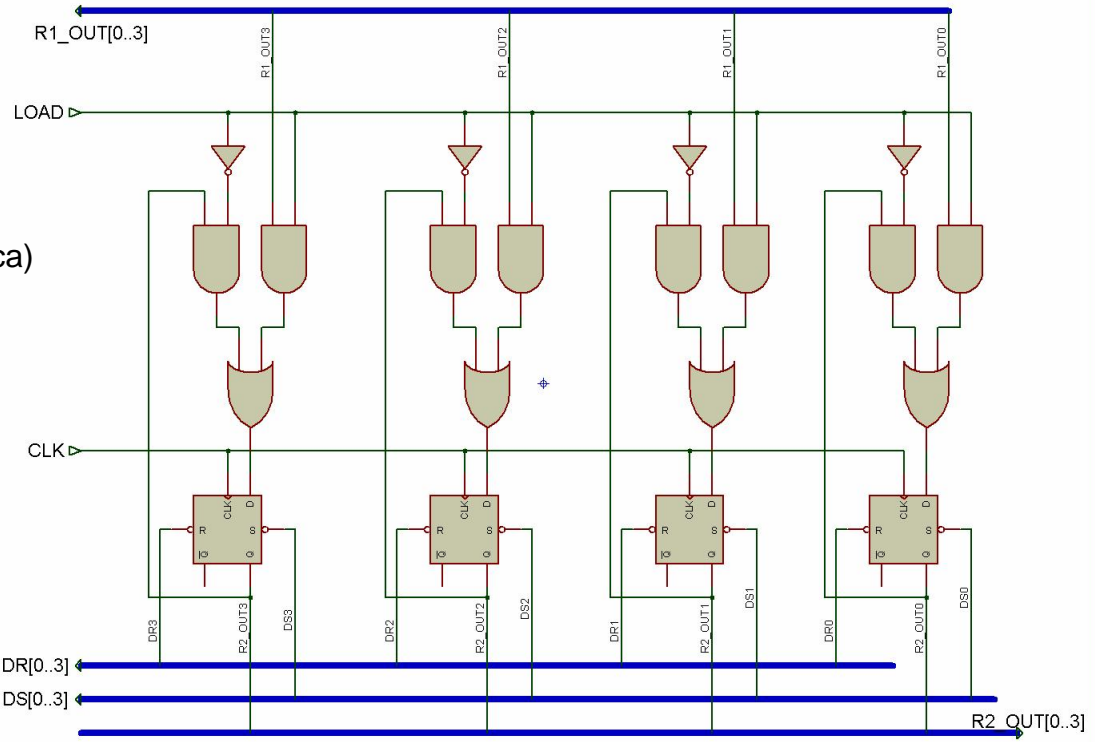


Fig. 2.4. - R2 register implemented with flip-flops D

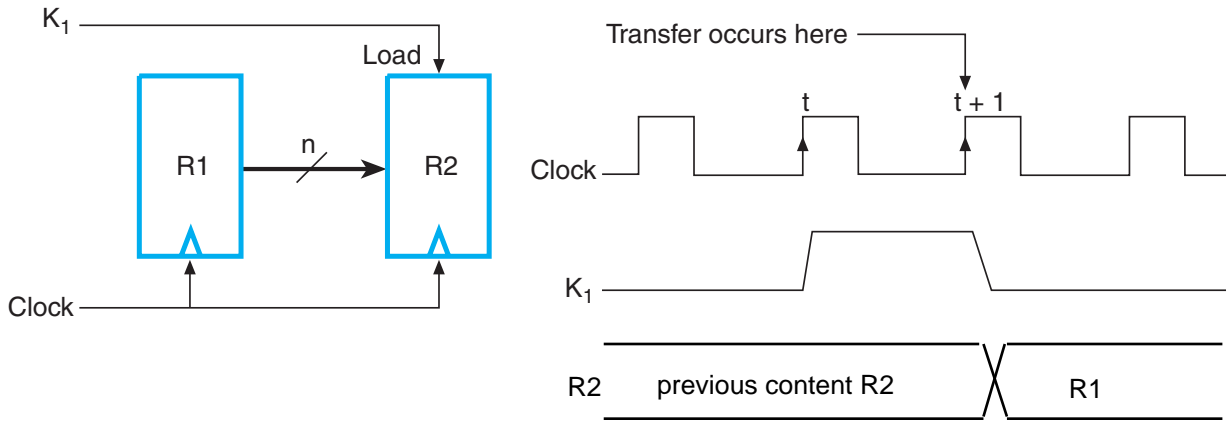


Fig. 2.5. Transfer from $R1$ to $R2$ when $K_1 = 1$


□ TABLE 2-1
Basic Symbols for Register Transfers

Symbol	Description	Examples
Letters (and numerals)	Denotes a register	$AR, R2, DR, IR$
Parentheses	Denotes a part of a register	$R2(1), R2(7:0), AR(L)$
Arrow	Denotes transfer of data	$R1 \leftarrow R2$
Comma	Separates simultaneous transfers	$R1 \leftarrow R2, R2 \leftarrow R1$
Square brackets	Specifies an address for memory	$DR \leftarrow M[AR]$

Table 2.1. Basic Symbols for Register Transfers


If (K1=1) then (R0 <- R1) else if (K2=1) then (R0 <- R2)

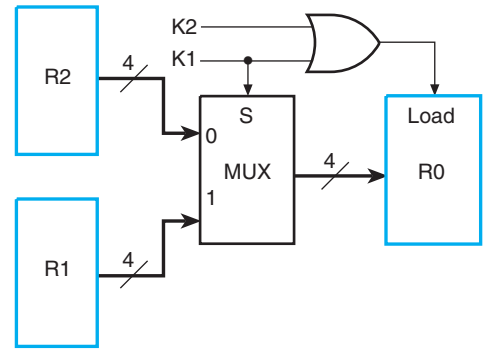K1: R0 <- R1, $\overline{K1}K2$: R0 <- R2




(a) Block diagram

K1	K2	Operation
0	0	No transf
0	1	R0 <- R2
1	0	R0 <- R1
1	1	R0 <- R1

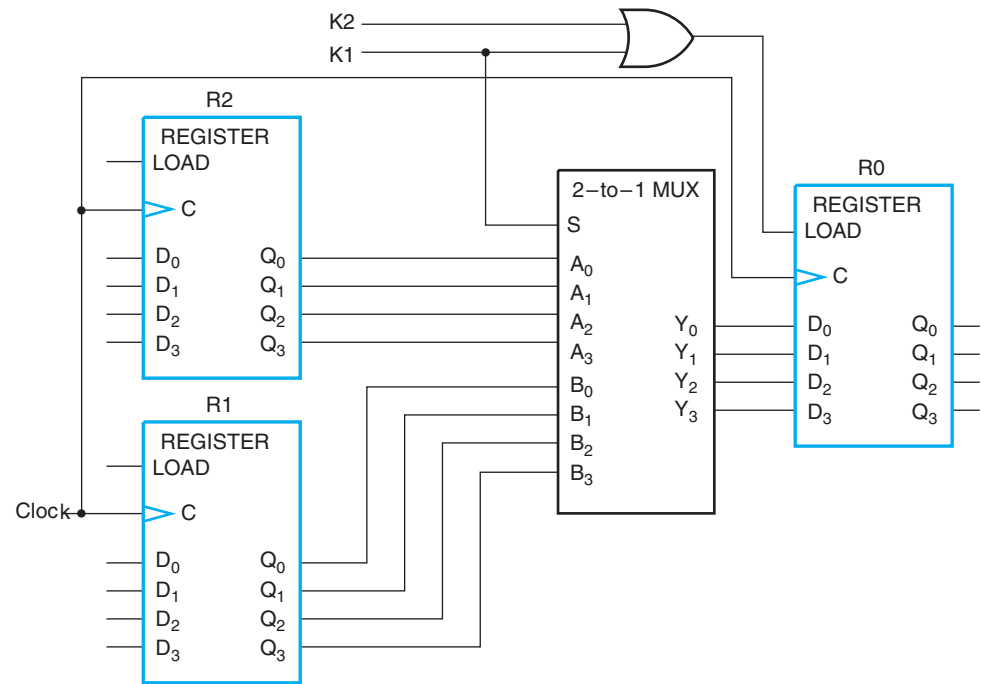


(b) Detailed logic

Fig 2.6. Use of Multiplexers to Select between Two Registers-Source

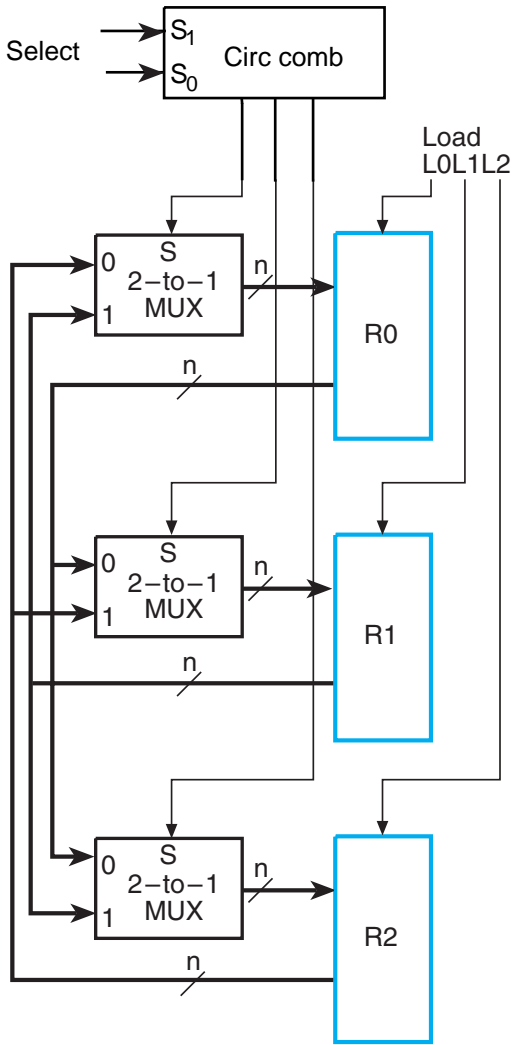

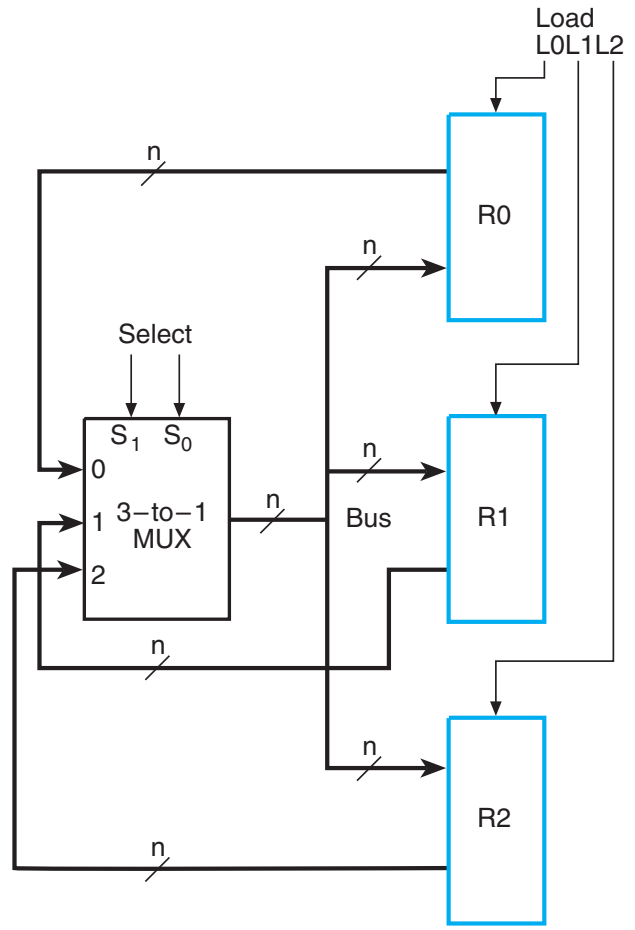(a) Dedicated multiplexers
 $3 [2n \text{ (AND)} + 1n \text{ (OR)}] = 9n$
 Simultaneous Transfers




(b) Single Bus
 $3n \text{ (AND)} + 1n \text{ (OR)} = 4n$
 Simplicity



Fig 2.7. Single Bus versus Dedicated Multiplexers

□ TABLE 2-2
Examples of Register Transfers Using the Single Bus in Figure 2-7(b)


Register Transfer	Select		Load		
	S1	S0	L2	L1	L0
$R0 \leftarrow R2$	1	0	0	0	1
$R0 \leftarrow R1, R2 \leftarrow R1$	0	1	1	0	1
$R0 \leftarrow R1, R1 \leftarrow R0$	Impossible				

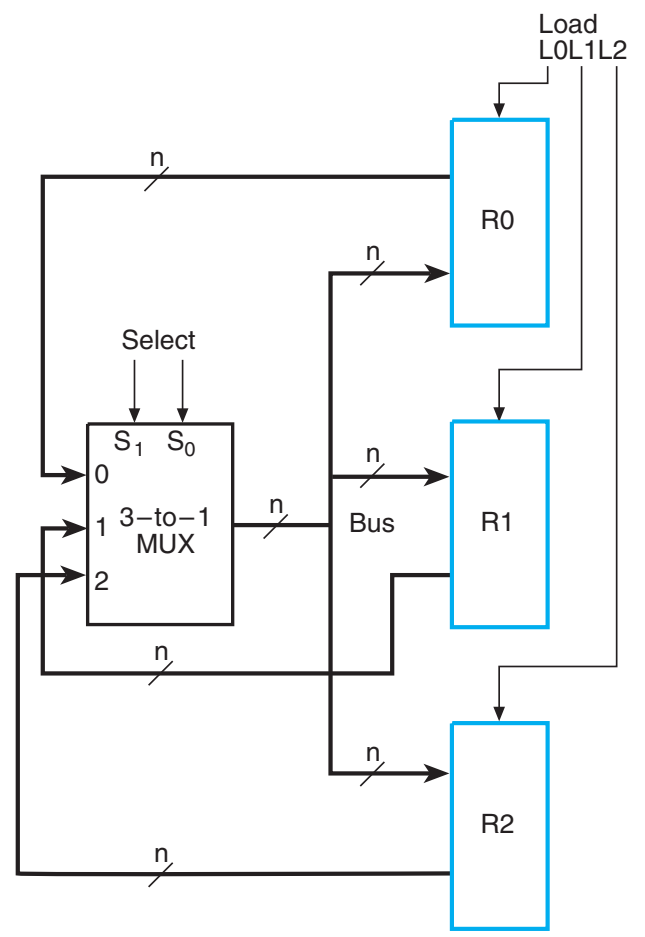Examples of Register Transfers Using the Single Bus in Figure 2-7(b)




  

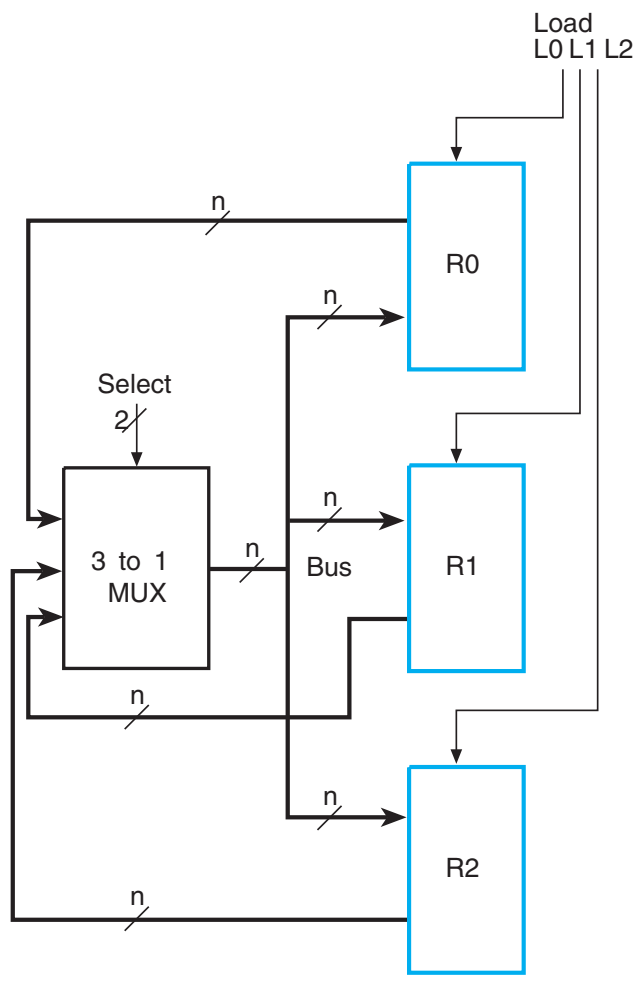(a) Register with bidirectional input-output lines and symbol



(b) Multiplexer bus

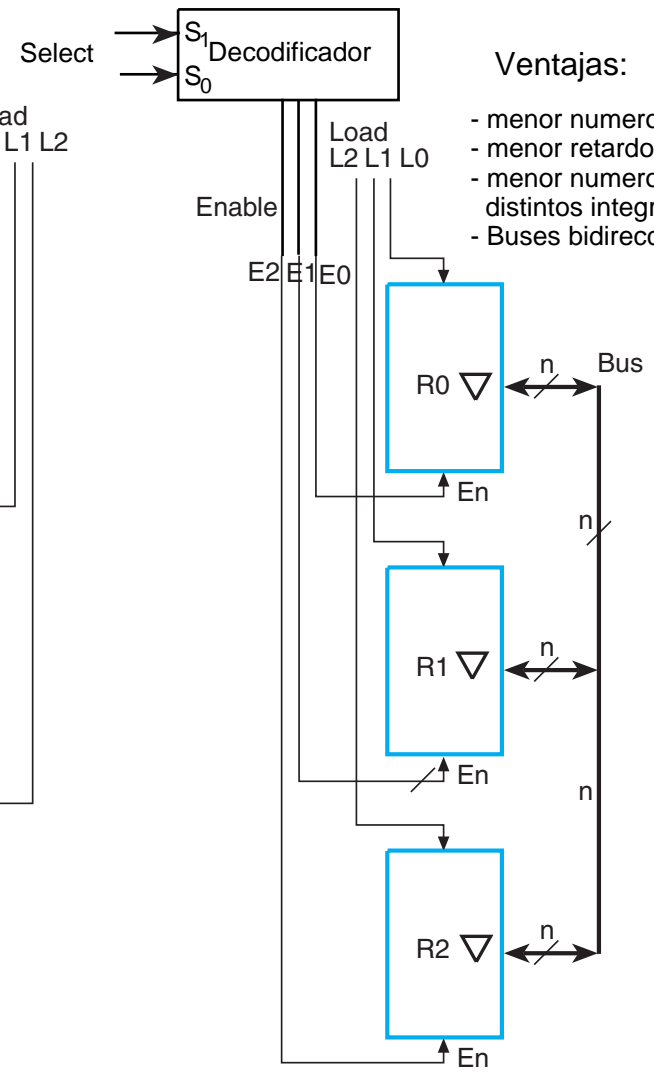

(c) Three-state bus using registers with bidirectional lines

Ventajas:

- menor numero de conexiones
- menor retardo de propagacion
- menor numero de pines si distintos integrados
- Buses bidireccionales

Fig 2.8. Three-State Bus versus Multiplexer Bus

Microoperacion: Operacion elemental ejecutada sobre datos almacenados en registros o en memoria

Tipos: Transferencia
 Aritmeticas
 Logicas
 Desplazamiento

□ TABLE 2-3
Arithmetic Microoperations

Symbolic designation	Description
$R0 \leftarrow R1 + R2$	Contents of $R1$ plus $R2$ transferred to $R0$
$R2 \leftarrow \overline{R2}$	Complement of the contents of $R2$ (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's complement of the contents of $R2$
$R0 \leftarrow R1 + \overline{R2} + 1$	$R1$ plus 2's complement of $R2$ transferred to $R0$ (subtraction)
$R1 \leftarrow R1 + 1$	Increment the contents of $R1$ (count up)
$R1 \leftarrow R1 - 1$	Decrement the contents of $R1$ (count down)

Table 2.3. Arithmetic Microoperations

$\overline{X}K1 : R1 \leftarrow R1+R2$

$XK1 : R1 \leftarrow R1+\overline{R2}+1$

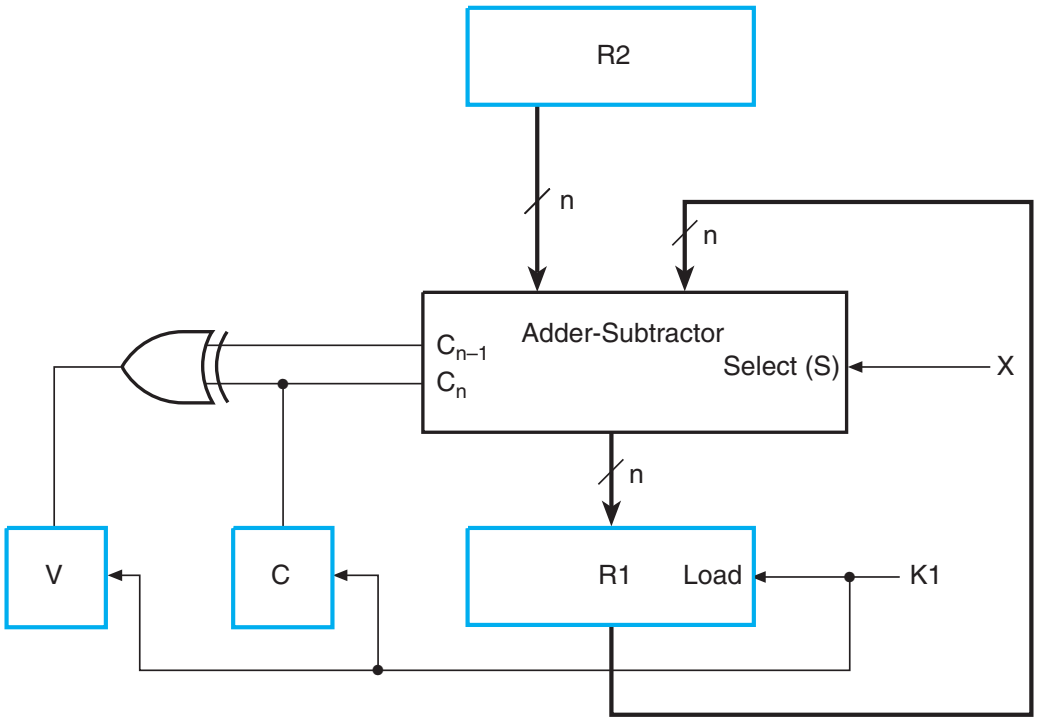


Fig 2.9. Implementation of Add and Subtract Microoperations

□ TABLE 2-4
Logic Microoperations

Symbolic designation	Description
$R0 \leftarrow \overline{R1}$	Logical bitwise NOT (1's complement)
$R0 \leftarrow R1 \wedge R2$	Logical bitwise AND (clears bits)
$R0 \leftarrow R1 \vee R2$	Logical bitwise OR (sets bits)
$R0 \leftarrow R1 \oplus R2$	Logical bitwise XOR (complements bits)

Table 2.4. Logic Microoperations

AND - Borrado Selectivo	$\begin{array}{r} 10101101 \\ \underline{00000000} \\ 00000000 \end{array}$	$\begin{array}{r} 10101011 \\ \underline{11111111} \\ 10101011 \end{array}$	R1 Datos	R2 Mascara	R1*R2
OR -Puesta a Set Selectiva	$\begin{array}{r} 10101101 \\ \underline{11111111} \\ 11111111 \end{array}$	$\begin{array}{r} 10101011 \\ \underline{00000000} \\ 10101011 \end{array}$	R1 Datos	R2 Mascara	R1+R2
XOR - Complemento Selectivo	$\begin{array}{r} 10101101 \\ \underline{00000000} \\ 10101101 \end{array}$	$\begin{array}{r} 10101011 \\ \underline{11111111} \\ 01010100 \end{array}$	R1 Datos	R2 Mascara	R1⊕R2

□ TABLE 2-5
Examples of Shifts

Type	Symbolic designation	Eight-bit examples	
		Source <i>R2</i>	After shift: Destination <i>R1</i>
shift left	$R1 \leftarrow sl R2$	10011110	00111100
shift right	$R1 \leftarrow sr R2$	11100101	01110010

Table 2.5. Examples of Shifts

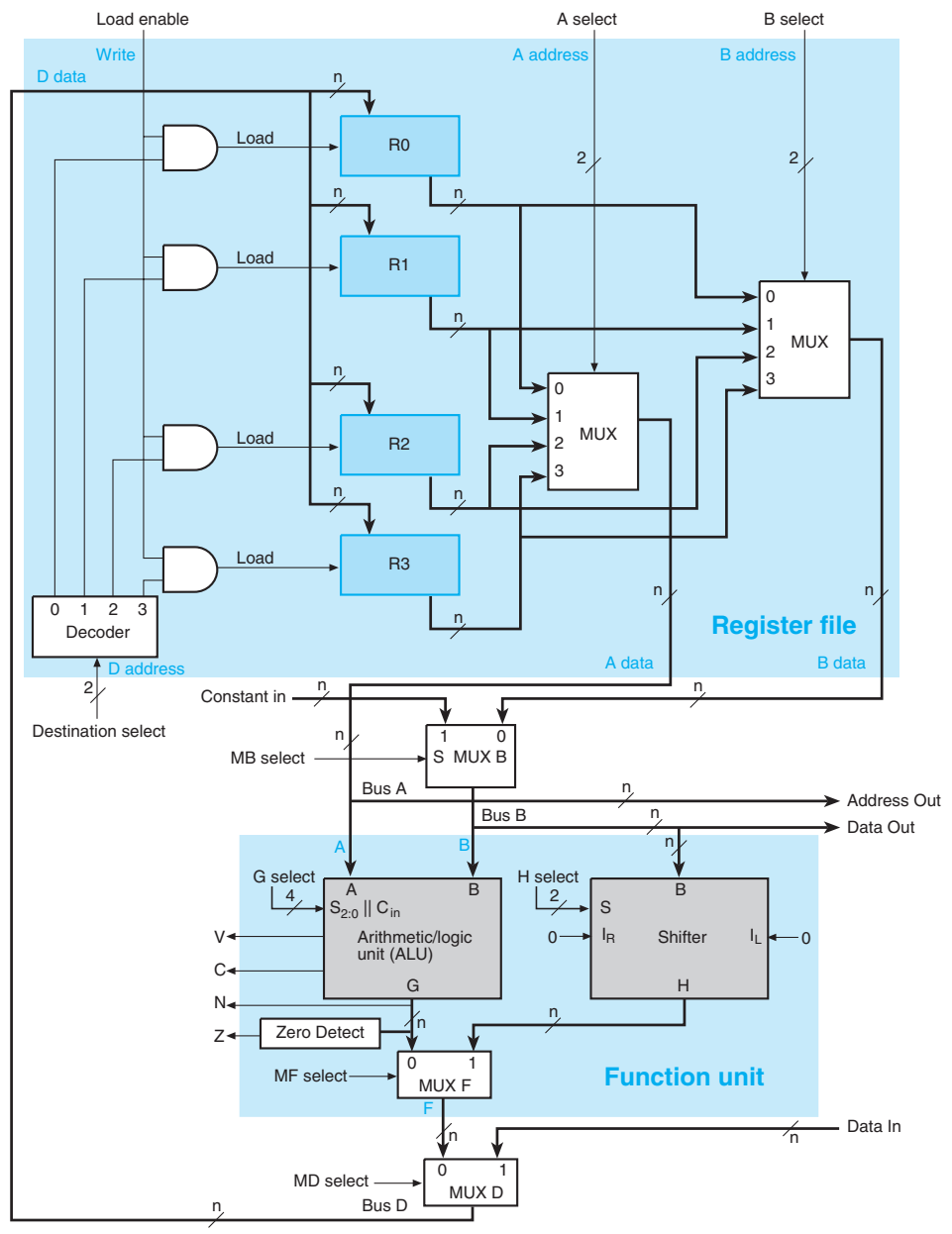


Fig 2.10. Block Diagram of a Datapath



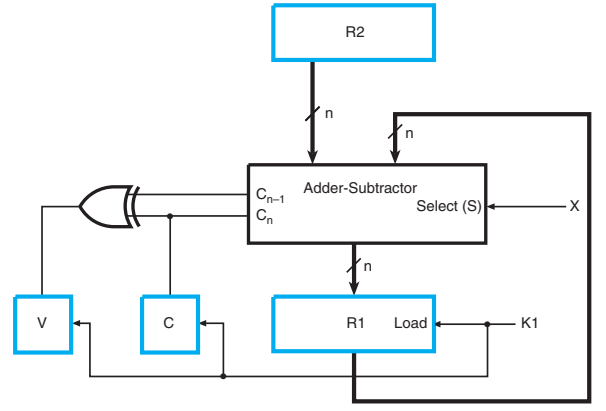
 


Fig 2.9. Implementation of Add and Subtract Microoperations

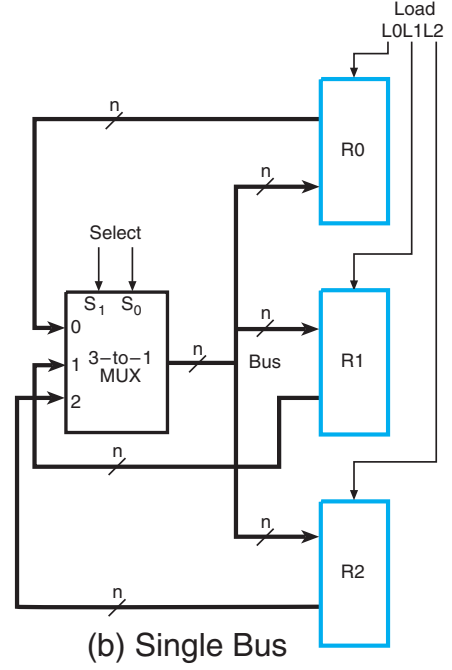

(b) Single Bus

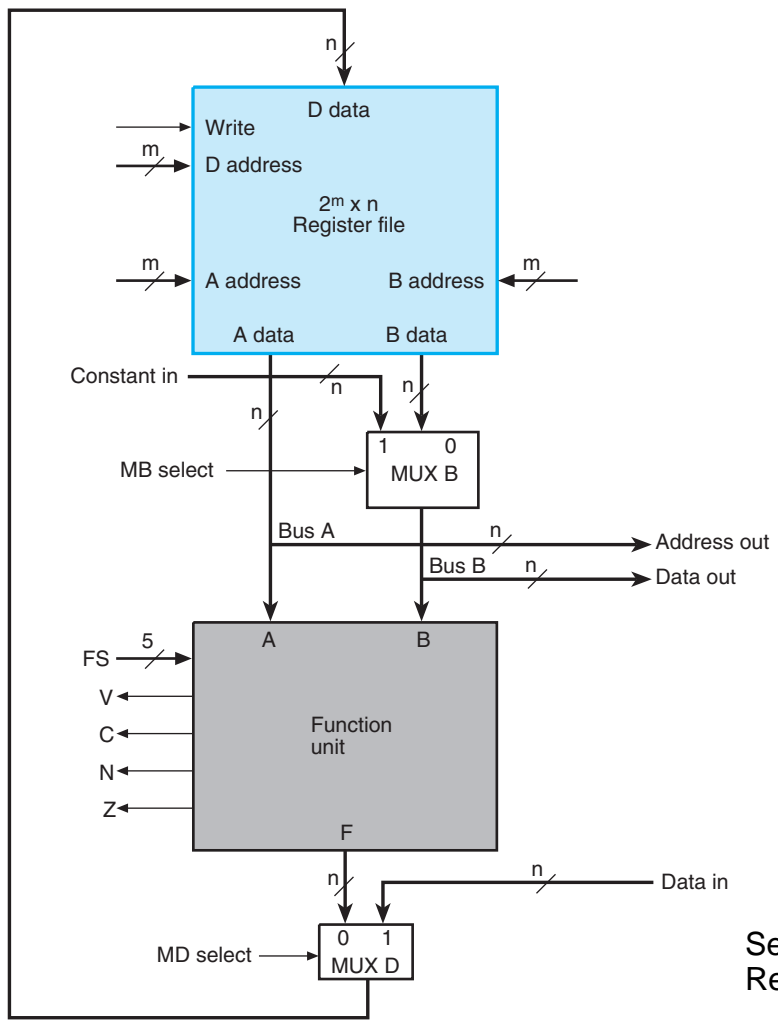

Entradas/Salidas Control:
 IN - Direccion A, B, D
 MB, MD, FS
 OUT - Bits Estado V, C, N, Z

Ejemplo: R1 <- R2 + R3

- 1 - Seleccion A R2 (direccion)
- 2 - Seleccion B R3 (direccion y MB)
- 3 - Seleccion FS (A+B)
- 4 - Seleccion MD (salida de unidad de funciones)
- 5 - Seleccion D R1 (direccion)
- 6 - Activacion Write

Señales activas comienzo del ciclo de reloj.
 Resultado aparece al comienzo del siguiente ciclo de reloj

Fig 2.11. Block Diagram of Datapath Using the Register File and Function Unit


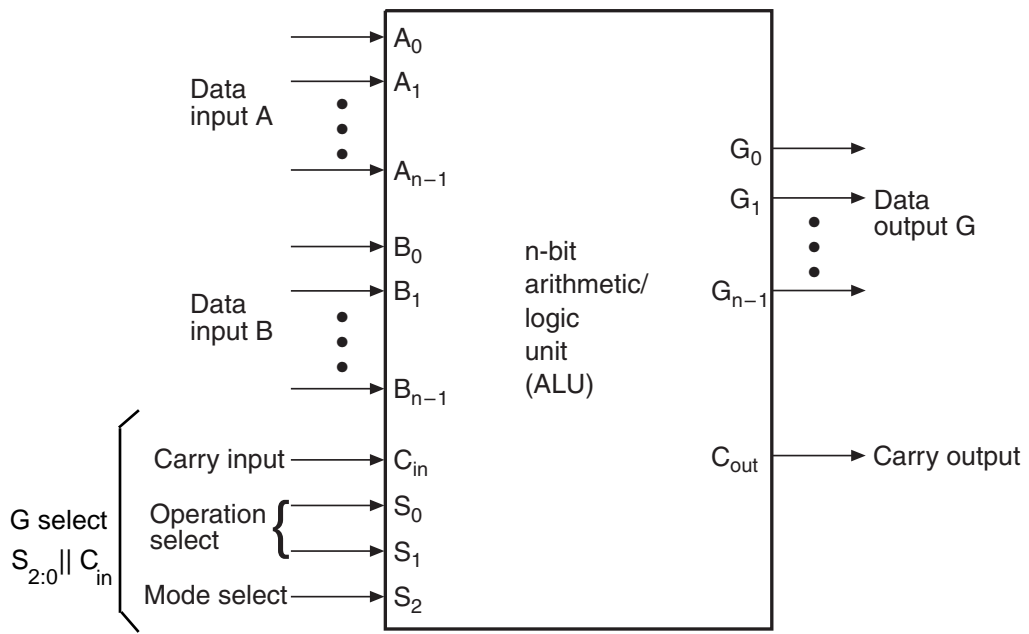


Fig 2.12. Symbol for an n -Bit ALU

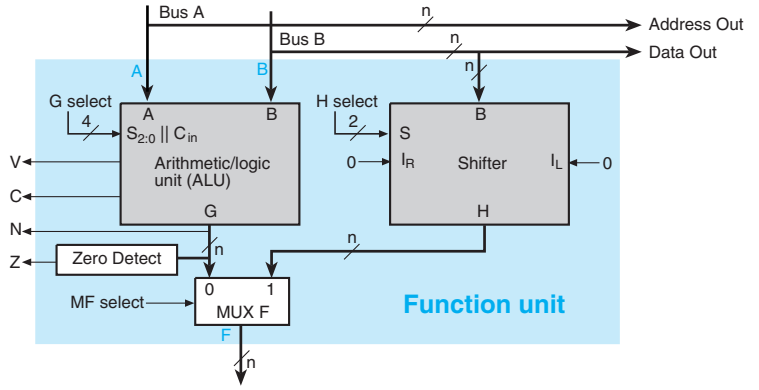

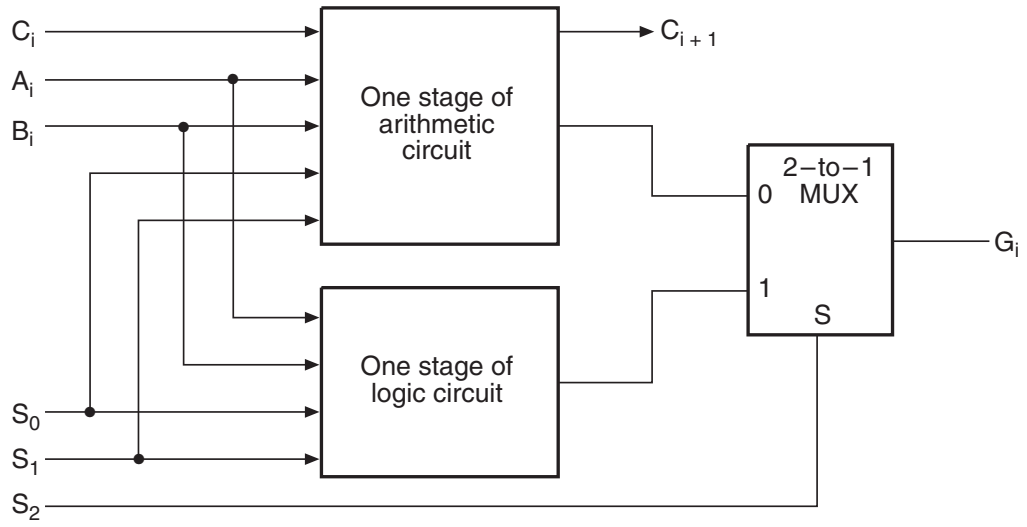


Fig 2.13. One Stage of ALU

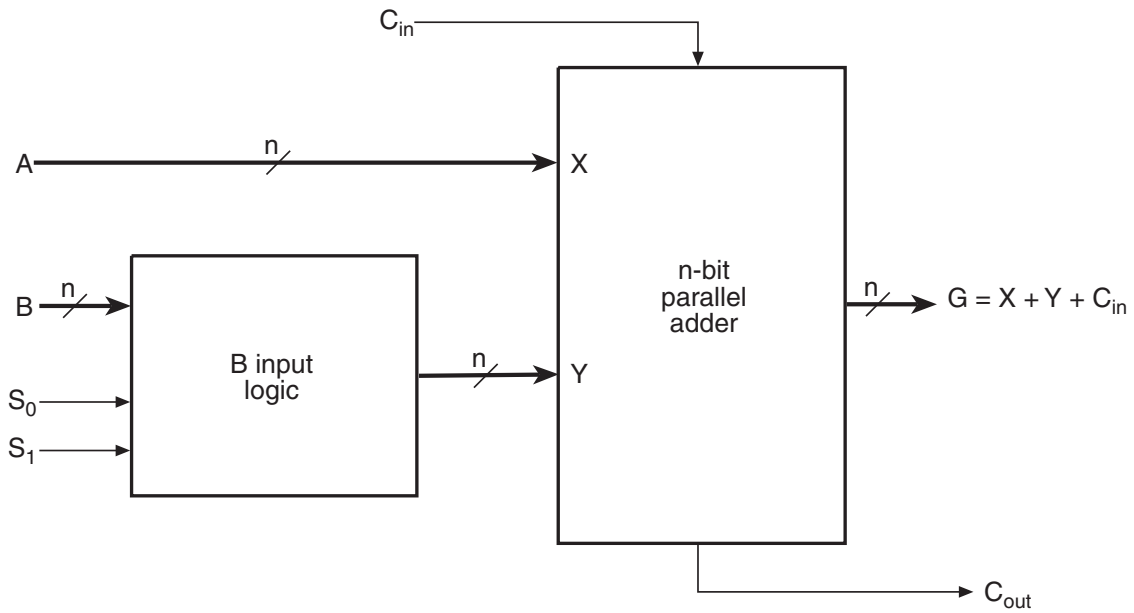


Fig. 2.14. Block Diagram of an Arithmetic Circuit


□ TABLE 2-6
Function Table for Arithmetic Circuit

Select		Input	$G = A + Y + C_{in}$	
S_1	S_0	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0's	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	\overline{B}	$G = A + \overline{B}$	$G = A + \overline{B} + 1$ (subtract)
1	1	all 1's	$G = A - 1$ (decrement)	$G = A$ (transfer)

Table 2.6. Function Table for Arithmetic Circuit

Inputs			Output	
S_1	S_0	B_i	Y_i	
0	0	0	0	$Y_i = 0$
0	0	1	0	
0	1	0	0	$Y_i = B_i$
0	1	1	1	
1	0	0	1	$Y_i = \bar{B}_i$
1	0	1	0	
1	1	0	1	$Y_i = 1$
1	1	1	1	

(a) Truth table

 

(b) Map Simplification:
 $Y_i = B_i S_0 + \bar{B}_i S_1$

Fig 2.15. B Input Logic for One Stage of Arithmetic Circuit


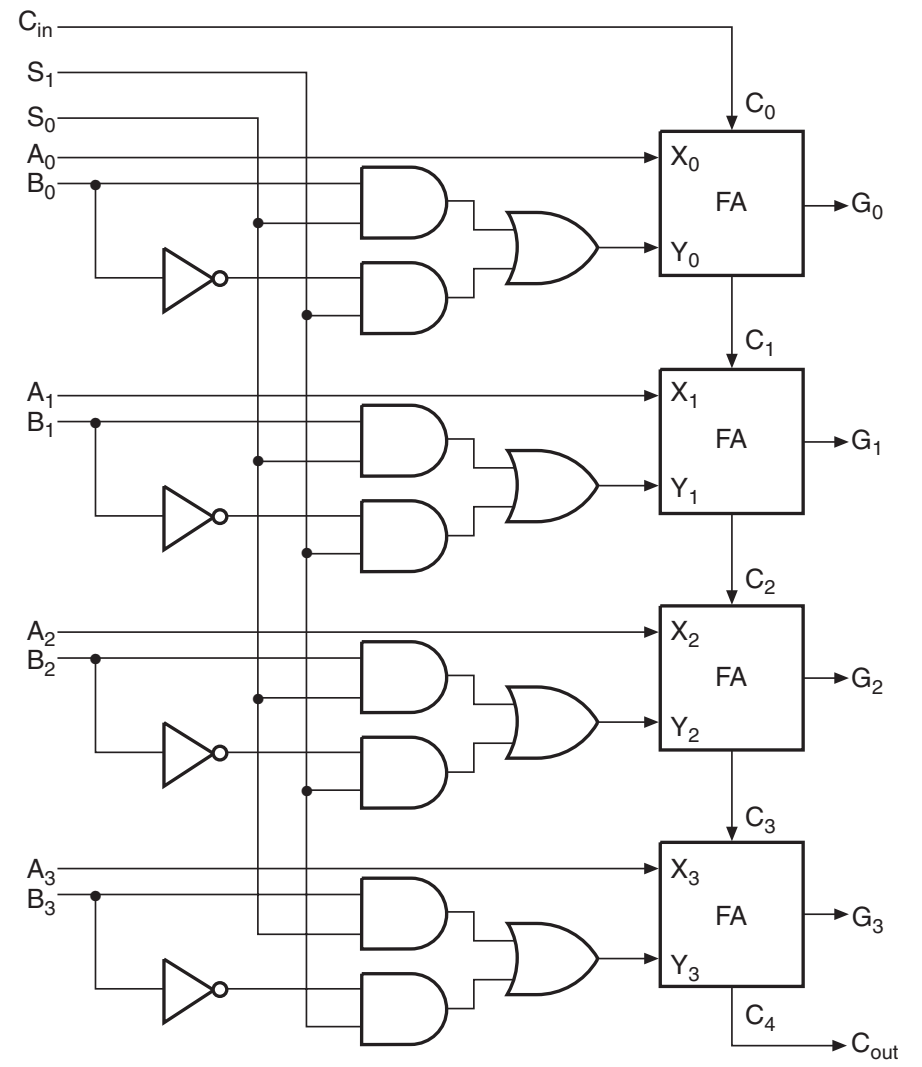


Fig 2.16. Logic Diagram of a 4-Bit Arithmetic Circuit

 

(a) Logic Diagram

S_1	S_0	Output	Operation
0	0	$G = A \wedge B$	AND
0	1	$G = A \vee B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT

(b) Function Table

Fig 2.17. One Stage of Logic Circuit

□ TABLE 2-7
Function Table for ALU

Operation Select				Operation	Function
S_2	S_1	S_0	C_{in}		
0	0	0	0	$G = A$	Transfer A
0	0	0	1	$G = A + 1$	Increment A
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + \underline{B} + 1$	Add with carry input of 1
0	1	0	0	$G = A + \underline{B}$	A plus 1's complement of B
0	1	0	1	$G = A + \underline{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement A
0	1	1	1	$G = A$	Transfer A
1	0	0	X	$G = A \wedge B$	AND
1	0	1	X	$G = A \vee B$	OR
1	1	0	X	$G = \underline{A} \oplus B$	XOR
1	1	1	X	$G = A$	NOT (1's complement)

Table 2.7. Function Table for ALU

 


Fig 2.18. 4-Bit Basic Shifter

TABLE 2-8

Select			Eight-bit examples		
S_1	S_0	Type		Source	After shift: Destination
0	0	no shift		10011110	10011110
0	1	shift right	sr	11100101	01110010
1	0	shift left	sl	10011110	00111100

Table 2.8. Examples of Shifts

 


Fig 2.19. 4-Bit Barrel Shifter

□ TABLE 2-9
Function Table for 4-Bit Barrel Shifter


Select		Output				Operation
S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀	
0	0	D ₃	D ₂	D ₁	D ₀	No rotation
0	1	D ₂	D ₁	D ₀	D ₃	Rotate one position
1	0	D ₁	D ₀	D ₃	D ₂	Rotate two positions
1	1	D ₀	D ₃	D ₂	D ₁	Rotate three positions

Table 2.9. Function Table for 4-Bit Barrel Shifter

□ TABLE 2-10
***G* Select, *H* Select, and *MF* Select Codes Defined
 in Terms of *FS* Codes**

FS					MF Select	G Select				H Select		Microoperation	
FS4	FS3	FS2	FS1	FS0		S2	S1	S0	Ci	S1	S0		
0	0	0	0	0	0	0	0	0	0	0	0	$F = A$	FS
0	0	0	0	1	0	0	0	0	1	0	0	$F = A + 1$	
0	0	0	1	0	0	0	0	1	0	0	0	$F = A + B$	FS4 ----- MF
0	0	0	1	1	0	0	0	1	1	0	0	$F = A + \overline{B} + 1$	
0	0	1	0	0	0	0	1	0	0	0	1	$F = A + \overline{B}$	FS3 ----- G3 (S2) ----- H1
0	0	1	0	1	0	0	1	0	1	0	1	$F = A + B + 1$	
0	0	1	1	0	0	0	1	1	0	0	1	$F = A - 1$	FS2 ----- G2 (S1) ----- H0
0	0	1	1	1	0	0	1	1	1	0	1	$F = A$	
0	1	0	0	0	0	1	0	0	0	1	0	$F = A \wedge B$	FS1 ----- G1 (S0)
0	1	0	1	0	0	1	0	1	0	1	0	$F = A \vee B$	FS0 ----- G0 (Cin)
0	1	1	0	0	0	1	1	0	0	1	0	$F = A \oplus B$	
0	1	1	1	0	0	1	1	1	0	1	0	$F = \overline{A}$	
1	0	0	0	0	1	0	0	0	0	0	0	$F = B$	
1	0	1	0	0	1	0	1	0	0	0	1	$F = sr B$	
1	1	0	0	0	1	1	0	0	0	0	1	$F = sl B$	

Table 2.10. *G* Select, *H* Select, and *MF* Select Codes Defined in Terms of *FS* Codes

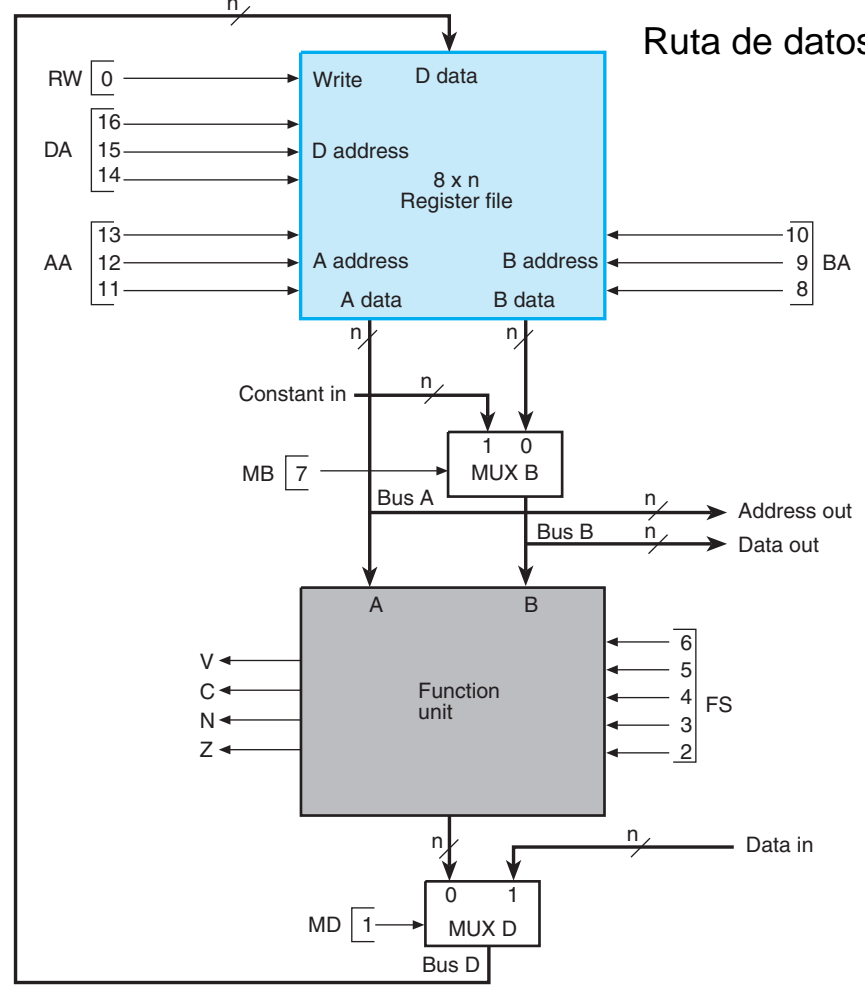

(a) Block Diagram

16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DA			AA			BA			M B		FS				M D	R W

(b) Control word

Fig. 2.20. Datapath with Control Variables

□ TABLE 2-11
Encoding of Control Word for the Datapath

DA, AA, BA		MB		FS		MD		RW	
Function	Code	Function	Code	Function	Code	Function	Code	Function	Code
<i>R0</i>	000	Register	0	$F = A$	00000	Function	0	No write	0
<i>R1</i>	001	Constant	1	$F = A + 1$	00001	Data In	1	Write	1
<i>R2</i>	010			$F = A + B$	00010				
<i>R3</i>	011			$F = A + B + 1$	00011				
<i>R4</i>	100			$F = A + \overline{B} + 1$	00100				
<i>R5</i>	101			$F = A + \overline{B}$	00101				
<i>R6</i>	110			$F = A - 1$	00110				
<i>R7</i>	111			$F = A$	00111				
				$F = A \wedge B$	01000				
				$F = A \vee B$	01010				
				$F = A \oplus B$	01100				
				$F = \overline{A}$	01110				
				$F = B$	10000				
				$F = sr B$	10100				
				$F = sl B$	11000				

Table 2.11. Encoding of Control Word for the Datapath

□ TABLE 2-12
Examples of Microoperations for the Datapath, Using Symbolic Notation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 + \overline{R3} + 1$	$R1$	$R2$	$R3$	Register	$F = A + \overline{B} + 1$	Function	Write
$R4 \leftarrow s1 R6$	$R4$	—	$R6$	Register	$F = s1 B$	Function	Write
$R7 \leftarrow R7 + 1$	$R7$	$R7$	—	Register	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	$R1$	$R0$	—	Constant	$F = A + B$	Function	Write
Data out $\leftarrow R3$	—	—	$R3$	Register	—	—	No Write
$R4 \leftarrow$ Data in	$R4$	—	—	—	—	Data in	Write
$R5 \leftarrow 0$	$R5$	$R0$	$R0$	Register	$F = A \oplus B$	Function	Write (Reset)

Table 2.12. Examples of Microoperations for the Datapath, Using Symbolic Notation

□ TABLE 2-13

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	00101	0	1
$R4 \leftarrow sl R6$	100	000	110	0	11000	0	1
$R7 \leftarrow R7 + 1$	111	111	000	0	00001	0	1
$R1 \leftarrow R0 + 2$	001	000	000	1	00010	0	1
$Data\ out \leftarrow R3$	000	000	011	0	00000	0	0
$R4 \leftarrow Data\ in$	100	000	000	0	00000	1	1
$R5 \leftarrow 0$	101	000	000	0	01100	0	1

Table 2.13. Examples of Microoperations from Table 2-12, Using Binary Control Words

Cuando la direccion de los operandos no es relevante se coloca a 000

Ejemplo, segunda microoperacion $R4 \leftarrow sl R6$, campo AA = 000


Inicialmente registros contienen su numero i.e. R3 contiene 03

Microoperations

- $R1 \leftarrow R2 - R3$
- $R4 \leftarrow sl R6$
- $R7 \leftarrow R7 + 1$
- $R1 \leftarrow R0 + 2$
- Data out $\leftarrow R3$
- $R4 \leftarrow$ Data in
- $R5 \leftarrow 0$

Escritura Registros en el ciclo siguiente

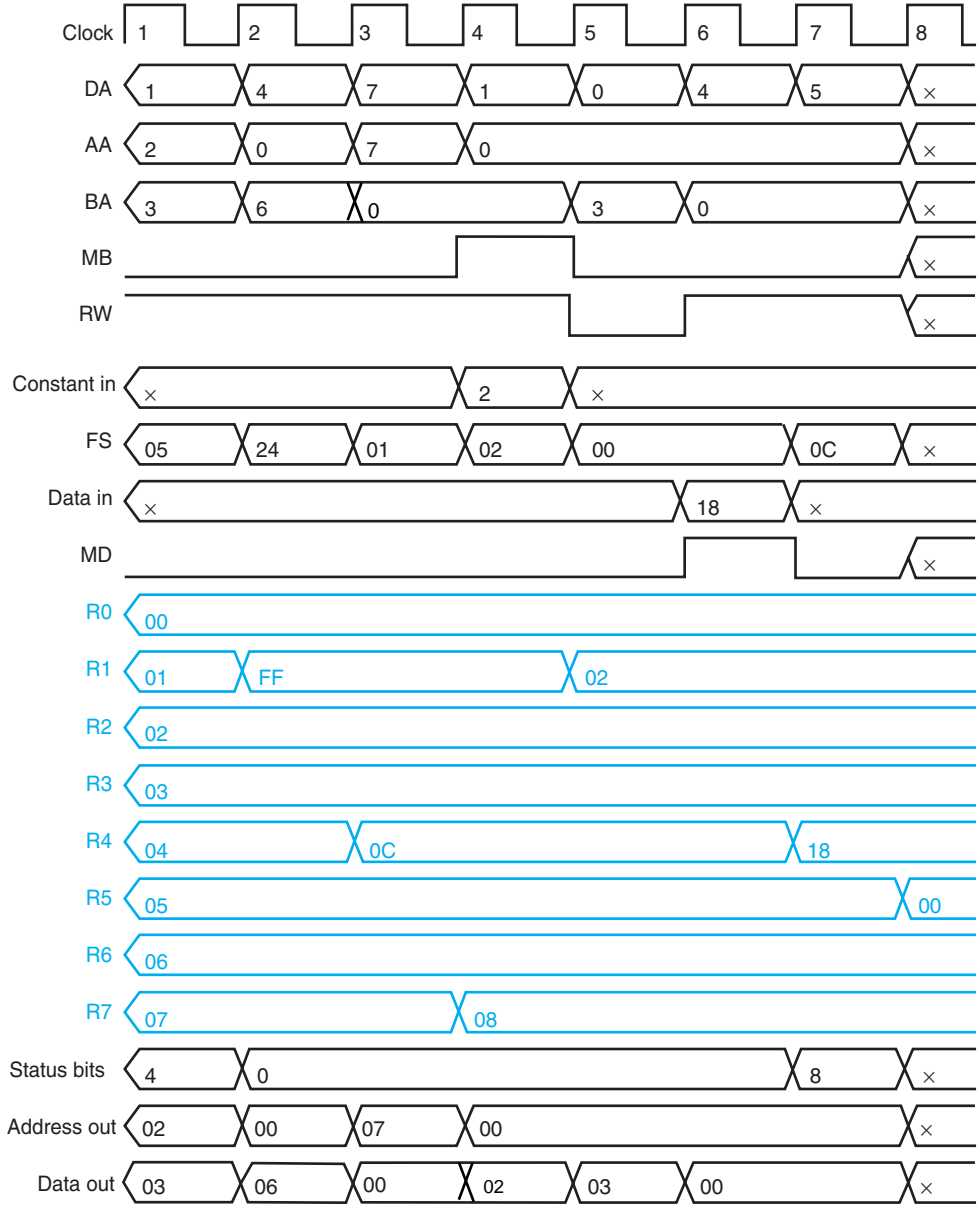bits estado y salida Unidad de Funciones en el mismo ciclo



ZNCV
Bus A
Bus B

Fig. 2.21. Simulation of the Microoperation Sequence in Table 3-13

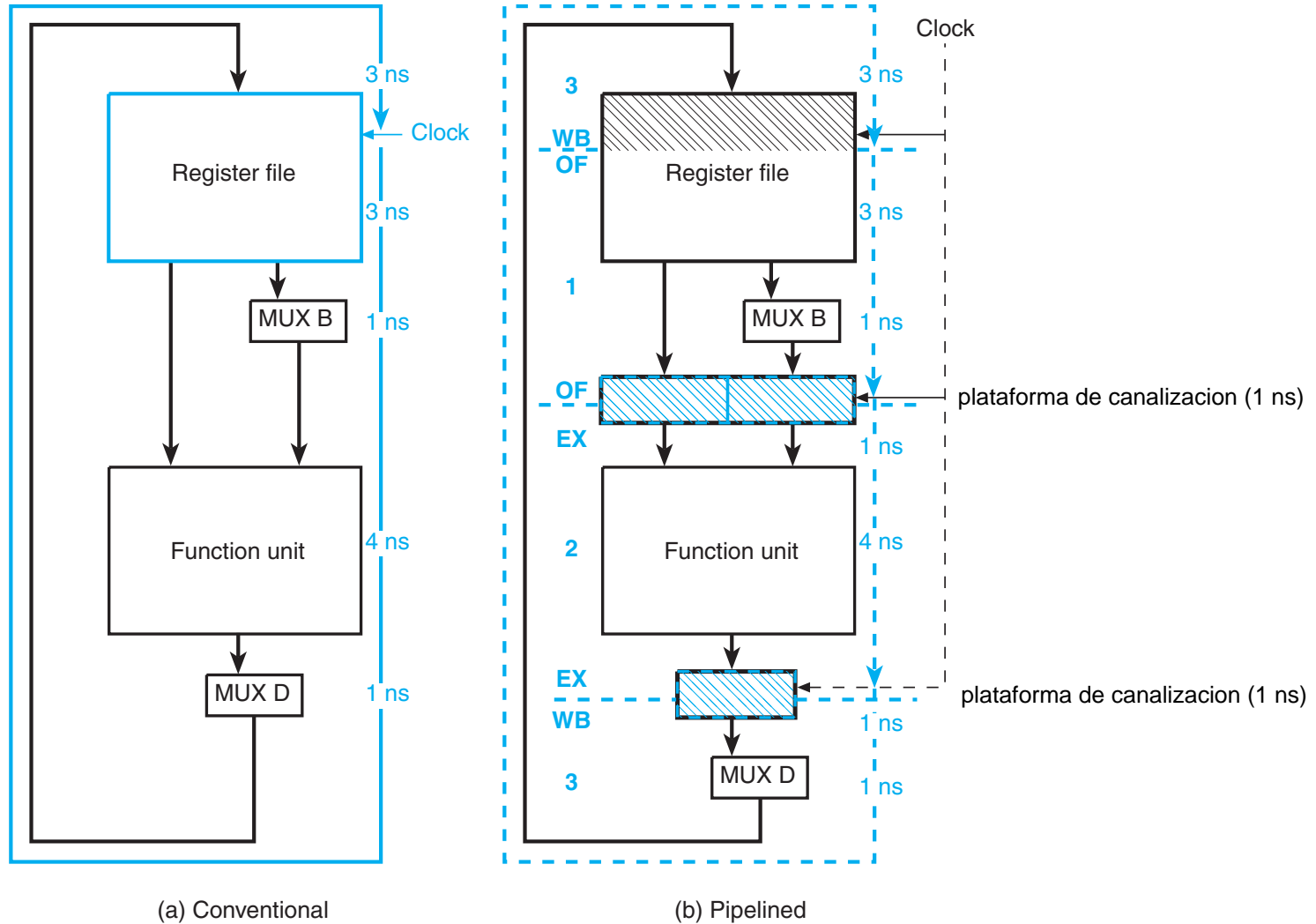
$T = 12 \text{ ns} \Rightarrow f = 83.3 \text{ MHz}$
 $T = 5 \text{ ns} \Rightarrow f = 200 \text{ MHz}$


Fig.2.22. Datapath Timing

1 operario: 1 pieza en 1 minuto

3 operarios: cada etapa 20 s => 3 piezas en 1 minuto!

 


Fig. 2.23. Assembly Line Analogy to Datapath Pipeline

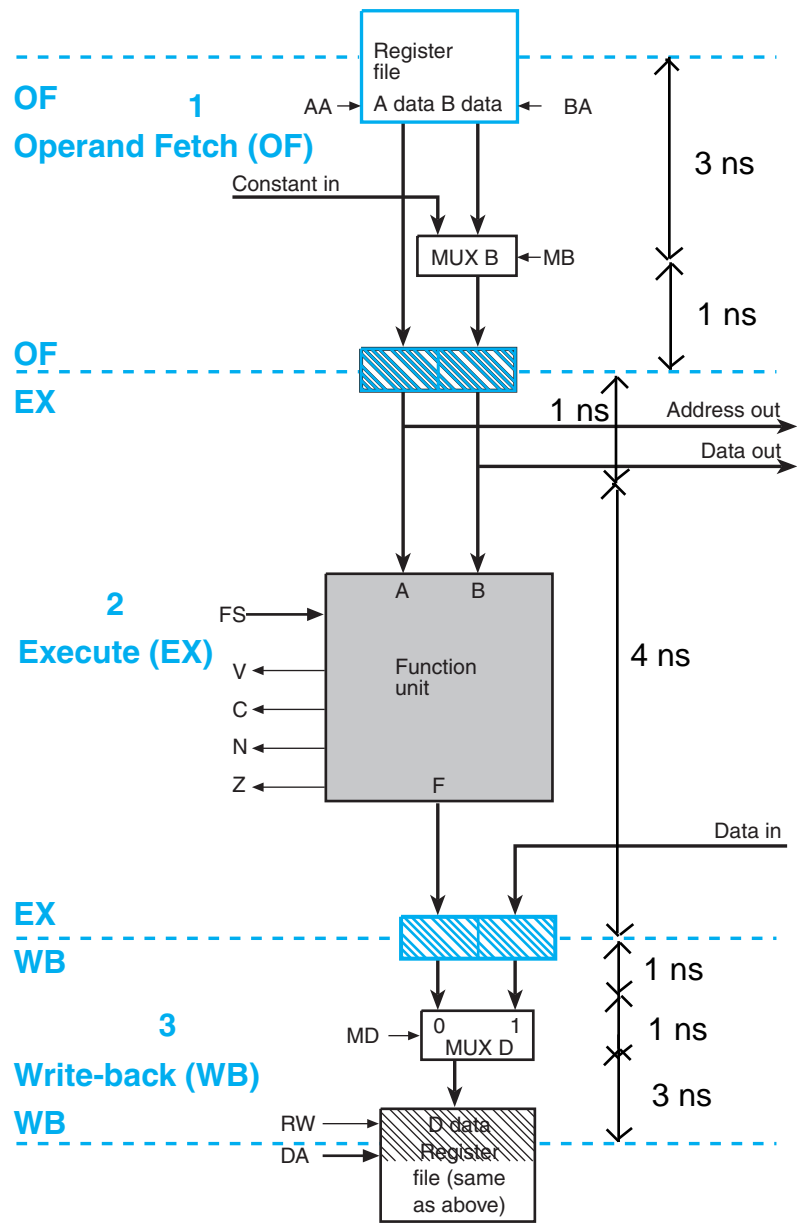


Fig.2.24. Block Diagram of Pipelined Datapath

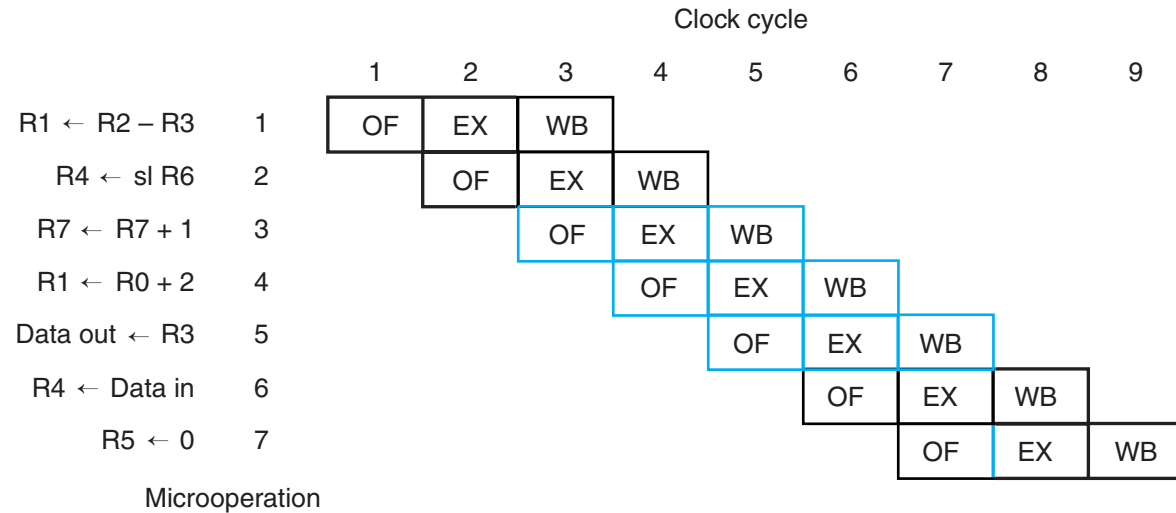


Fig. 2.25. Pipeline Execution Pattern for Microoperation Sequence in Table 3-13

{	sin pipeline: 7 operaciones en 7 ciclos (12 ns): $7 \times 12 = 84$ ns	}	$84 / 45 = 1.87$
	con pipeline: 7 operaciones en 9 ciclos (5 ns): $9 \times 5 = 45$ ns		
{	sin pipeline: 5 operaciones en 5 ciclos (12 ns): $5 \times 12 = 60$ ns	}	$60 / 25 = 2.4$
	con pipeline: 5 operaciones en 5 ciclos (5 ns): $5 \times 5 = 25$ ns		